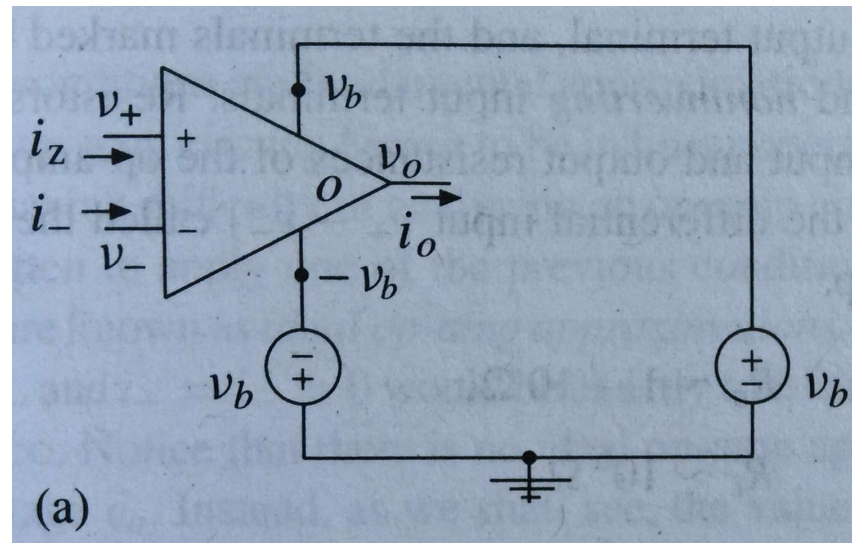


# Chapter 3



## Circuit for Signal Processing

## 3.1 op-amp & signal arithmetic



- Four inputs: terminals with node voltage  $V_+$  and  $V_-$ ; terminals with biasing voltage  $V_b$  and  $-V_b$  ( $V_b$  is positive)
- One output: terminal with node voltage  $V_o$




- $V_o = A(V_+ - V_-) - R_o i_o$

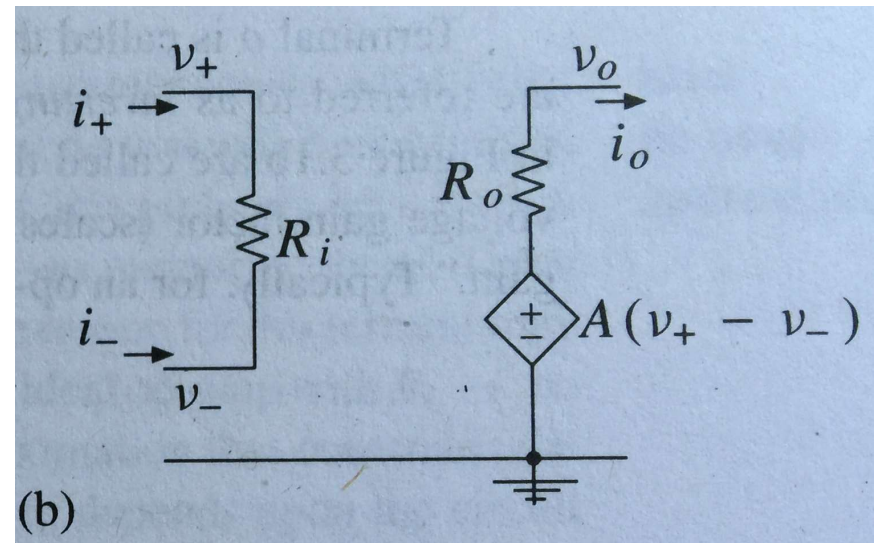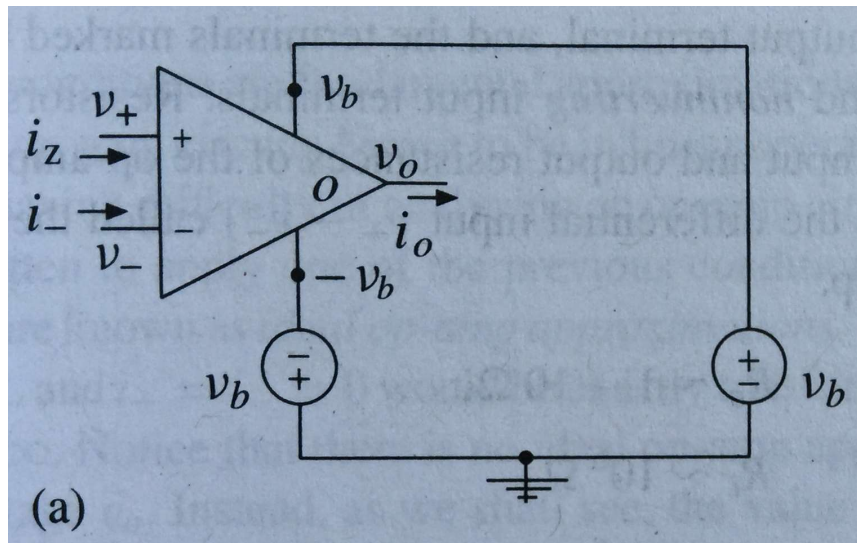

- $V_o = A(V_+ - V_-) - R_o i_o$
- $|V_o|$  cannot be larger than  $V_b$

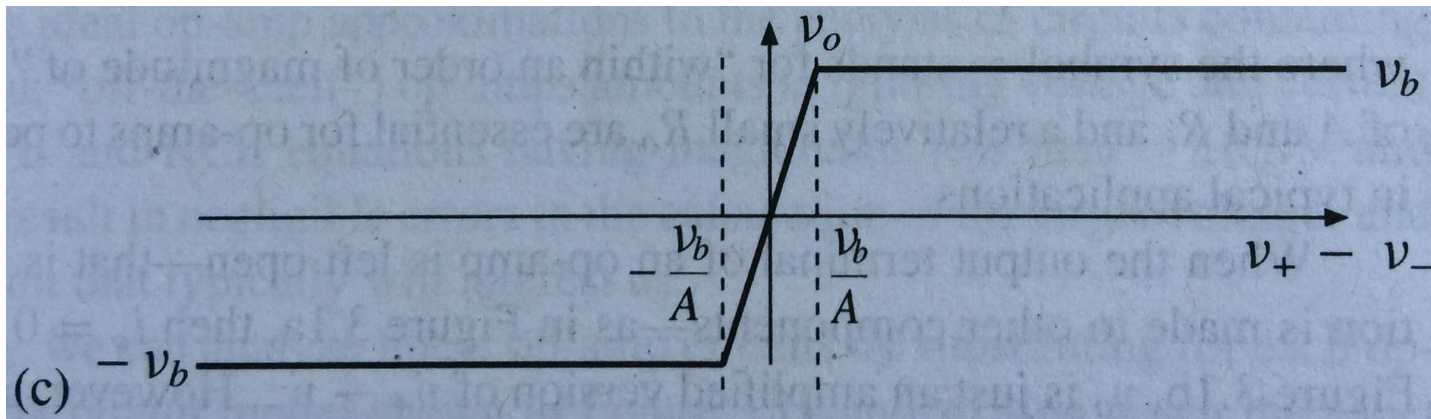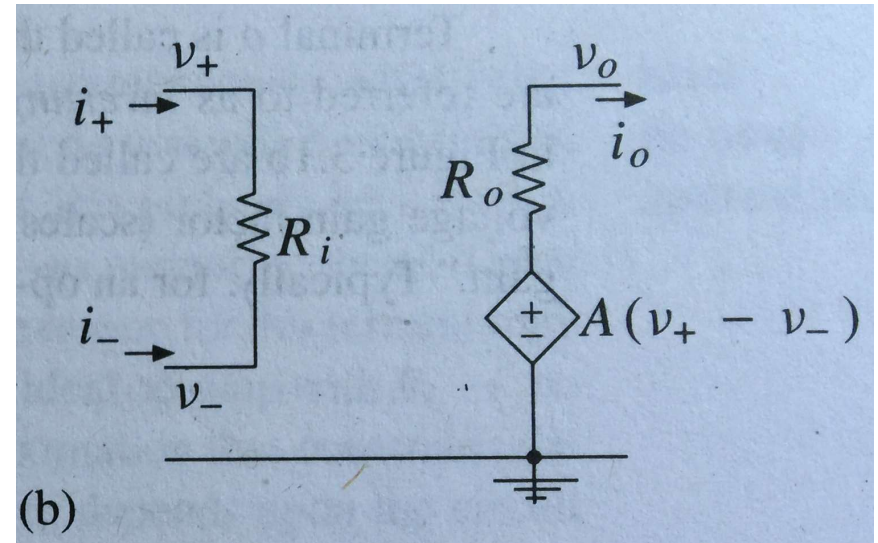

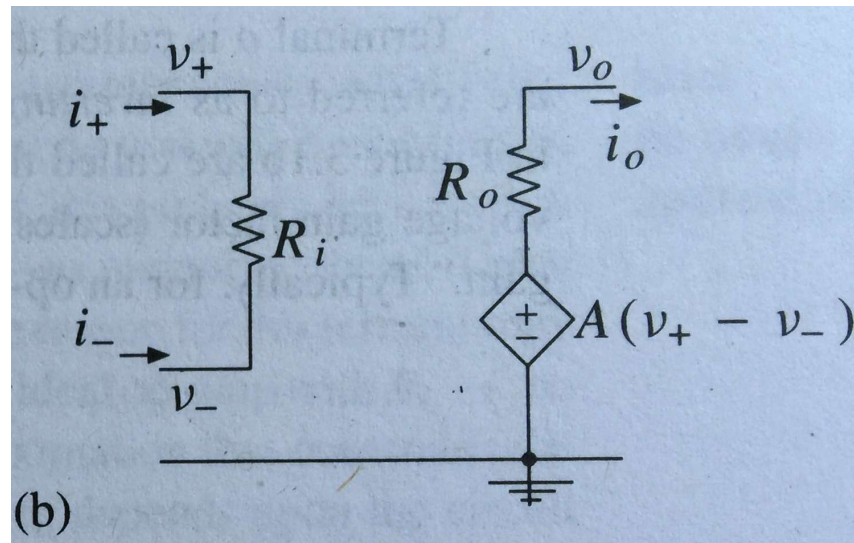

$$R_o \sim 1 - 10 \, \Omega$$

$$R_i \sim 10^6 \, \Omega$$


$$A \sim 10^6$$



$$R_o = 0 \, \Omega$$

$$R_i \rightarrow \infty \, \Omega$$

$$A \rightarrow \infty$$

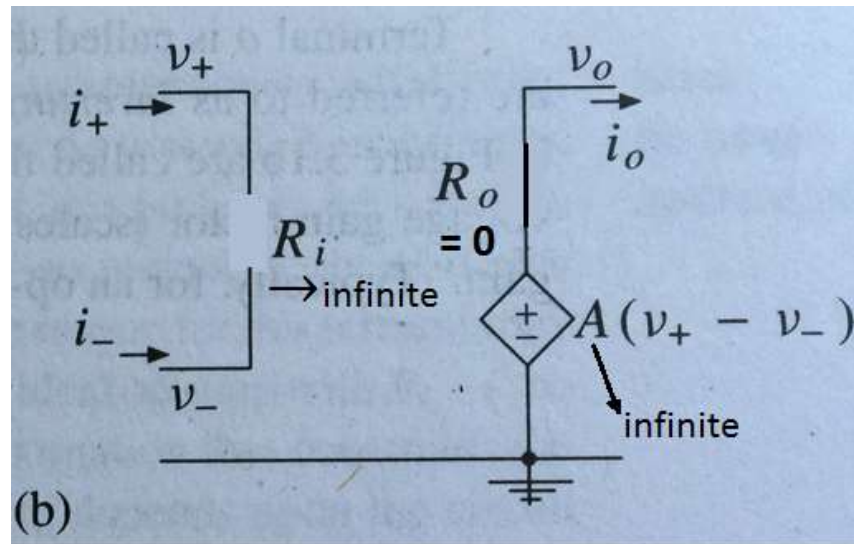

$$R_o \sim 1 - 10 \, \Omega$$

$$R_i \sim 10^6 \, \Omega$$


$$A \sim 10^6$$



$$R_o = 0 \, \Omega$$


$$R_i \rightarrow \infty \, \Omega$$

$$A \rightarrow \infty$$

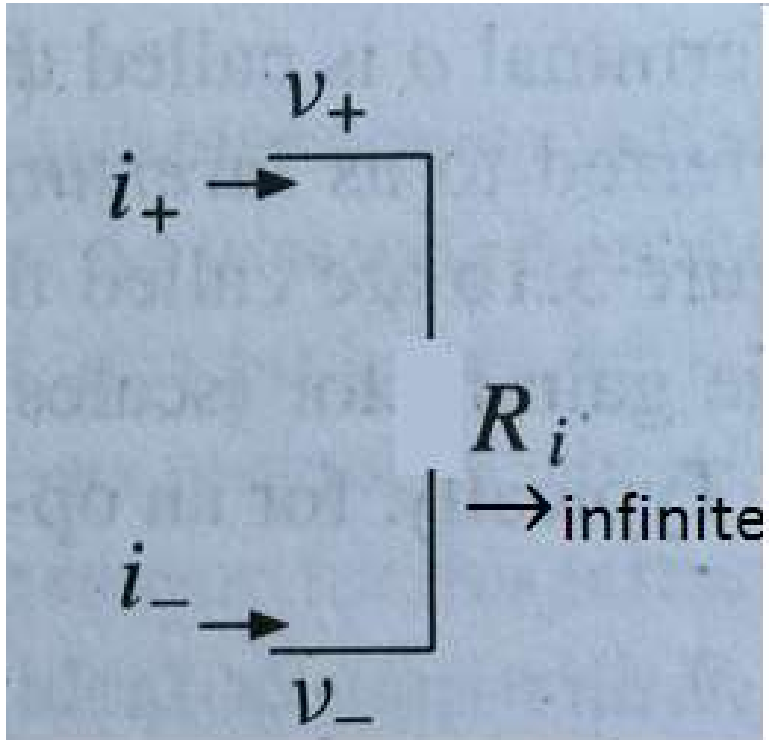

- $i_+ = i_- = 0$
- $V_+ = V_-$

- Voltage follower

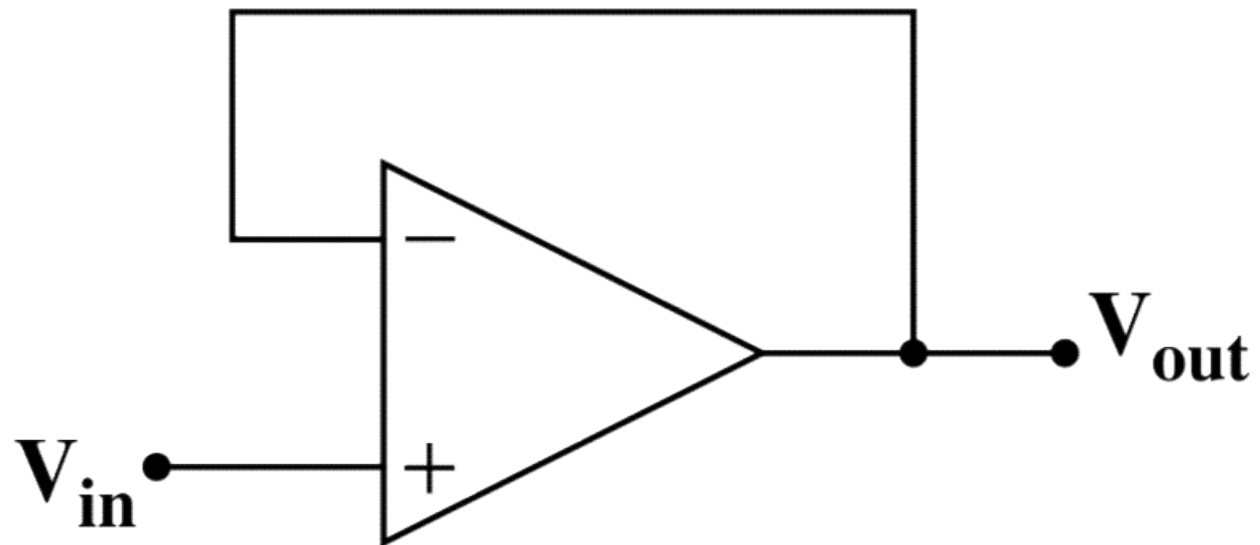




- Voltage follower


- $V_+ = V_-$

- $V_{in} = V_{out}$

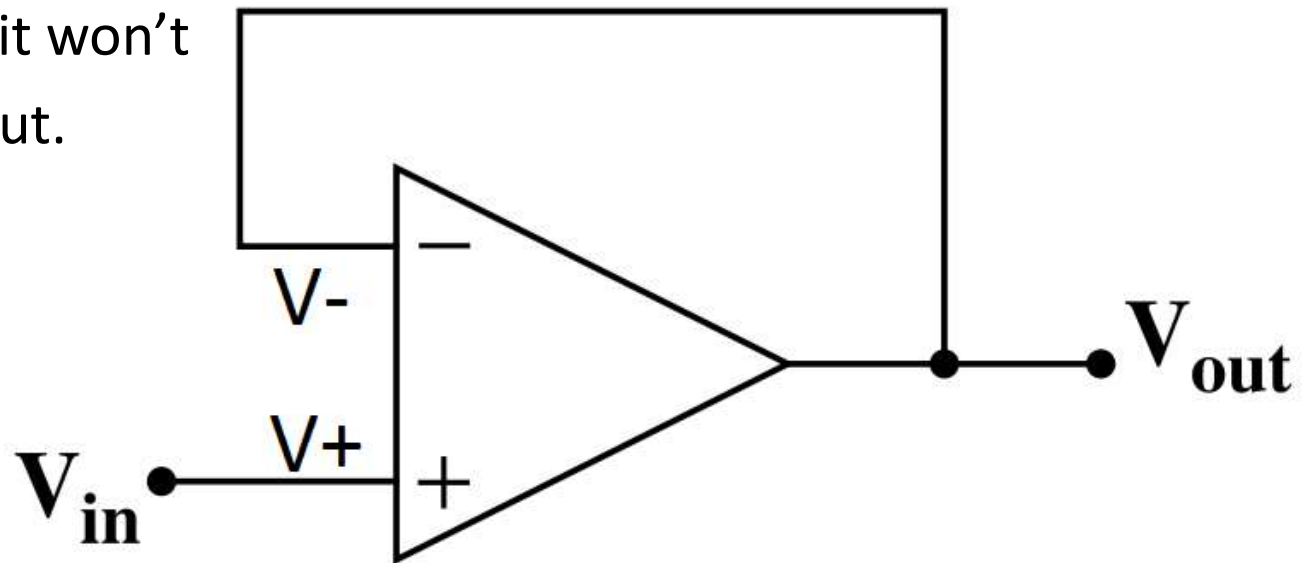- The output side circuit won't affect the voltage output.



- Noninverting amplifier

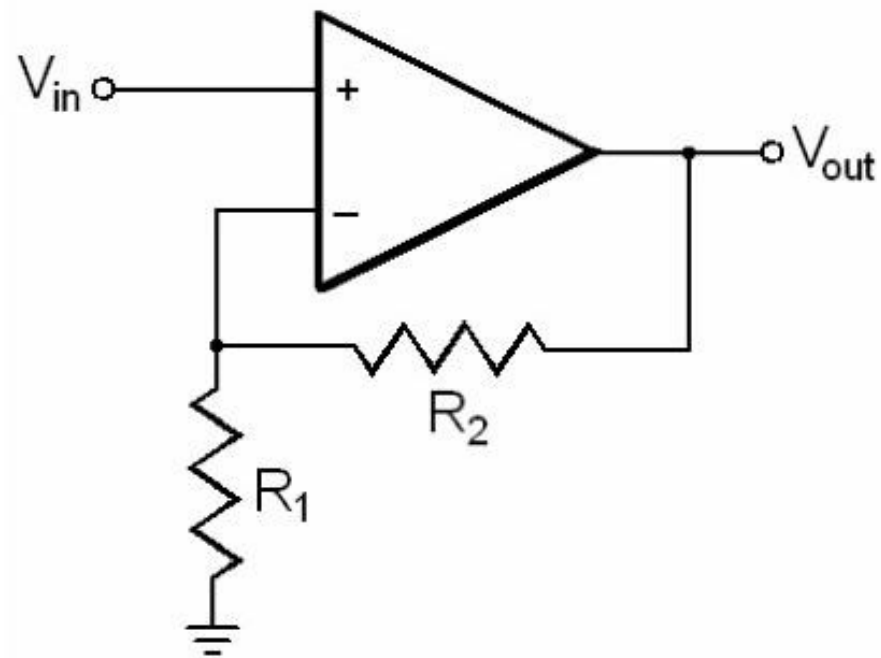

- Noninverting amplifier


- $V_+ = V_- = V_{in}$

- $i_- = 0$


- According to KCL,

$$\frac{V_-}{R_1} = \frac{V_{out} - V_-}{R_2}$$

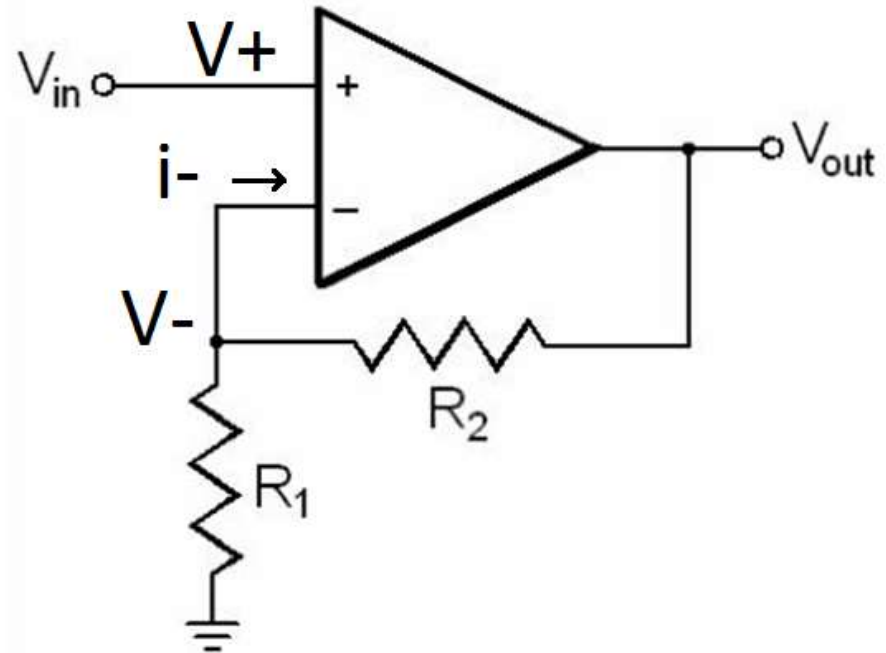
- $V_{out} = \left(1 + \frac{R_2}{R_1}\right) V_{in}$



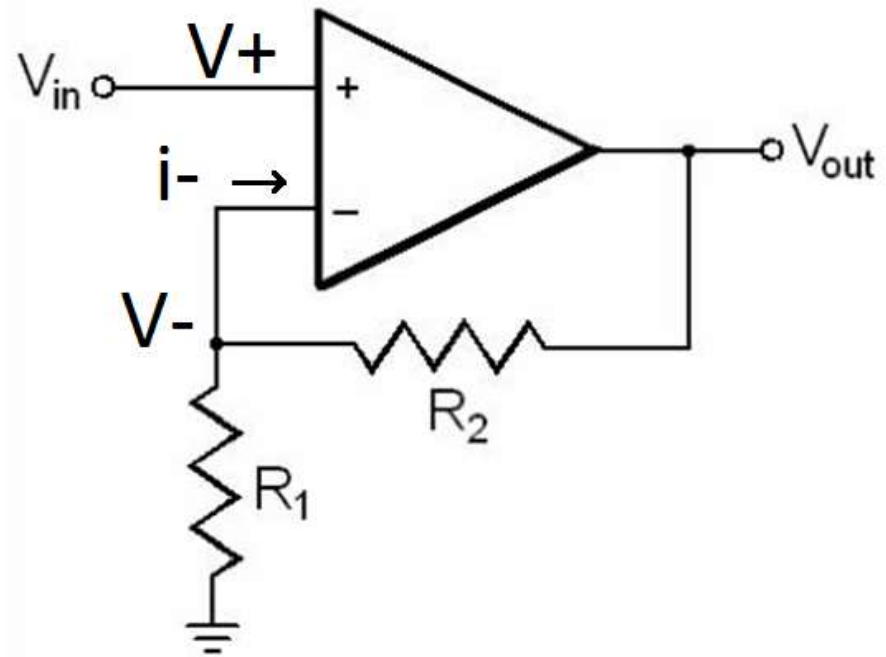- Noninverting amplifier
- Negative feedback  
Connecting the output of an op-amp to its inverting (-) input is called *negative feedback*.




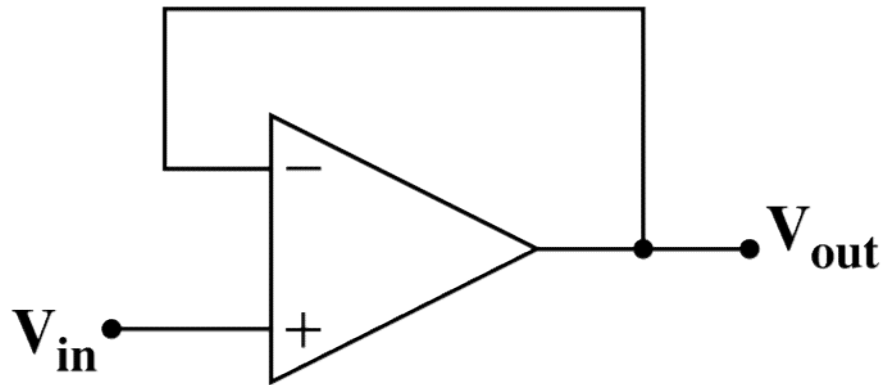- Why negative feedback?
- When the output of an op-amp is *directly* connected to its inverting (-) input, a *voltage follower* will be created. An op-amp with negative feedback will try to drive its output voltage to whatever level necessary so that the differential voltage between the two inputs is practically zero.



$$V_o = A(V_+ - V_-) - R_o i_o$$

- Inverting amplifier

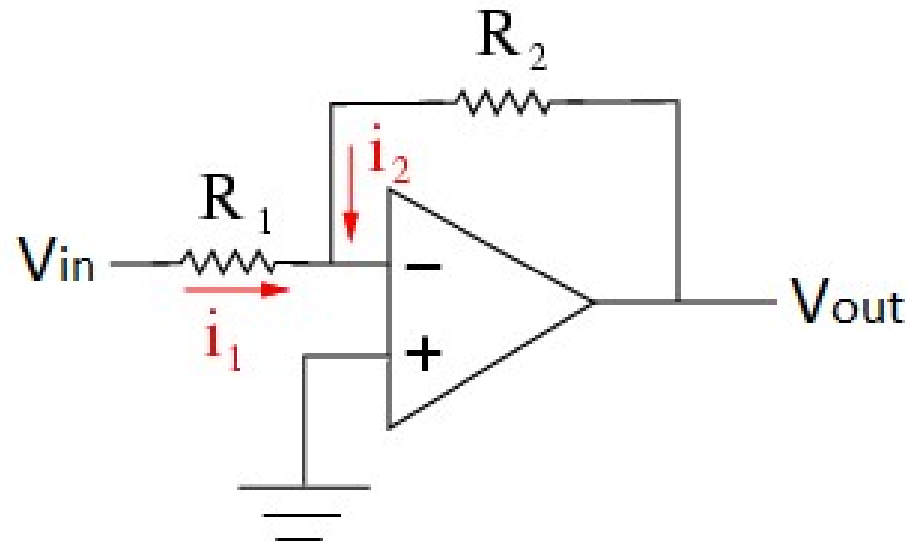

- Inverting amplifier


$$i_1 + i_2 = 0 \quad V_+ = V_- = 0$$

$$\frac{V_{in}}{R_1} + \frac{V_{out}}{R_2} = 0$$

$$V_{out} = -\frac{R_2}{R_1} V_{in}$$


- Voltage gain
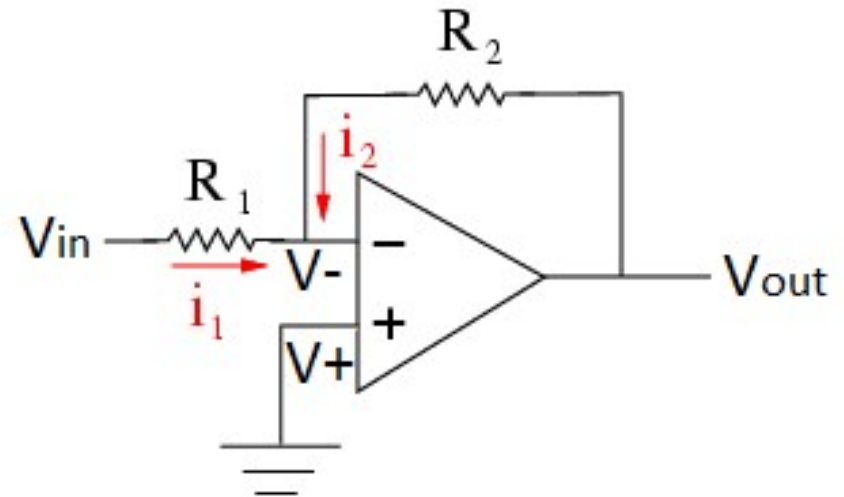
$$G = \frac{V_{out}}{V_{in}} = -\frac{R_2}{R_1}$$




- Sum and difference calculators

sum

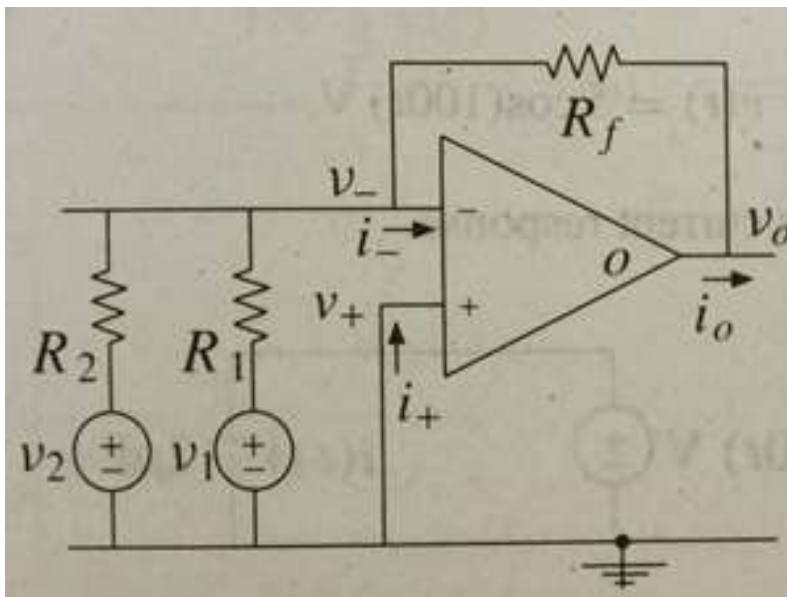

difference

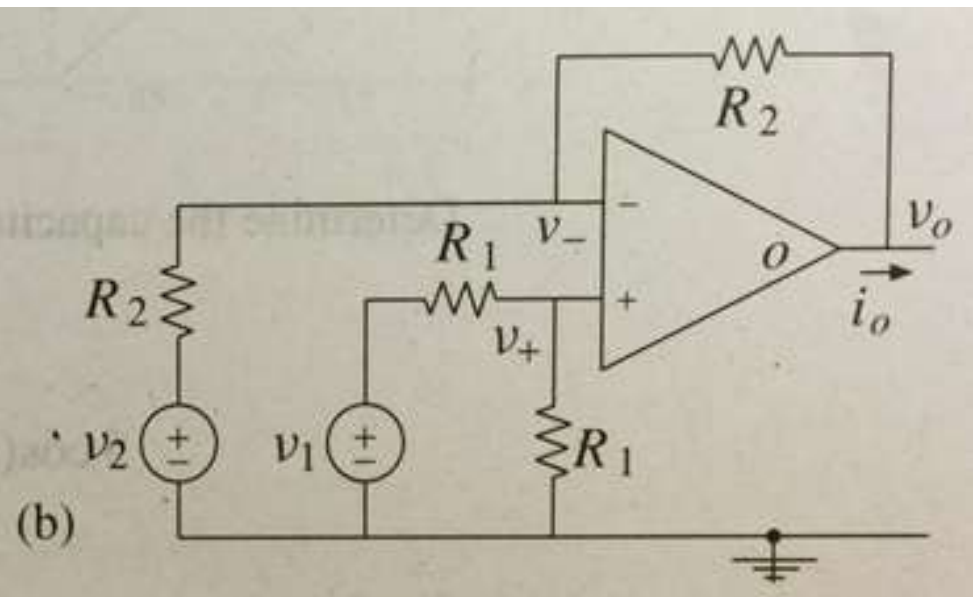




## 3.2 Differentiators and Integrators

- Capacitor and inductor


Capacitor

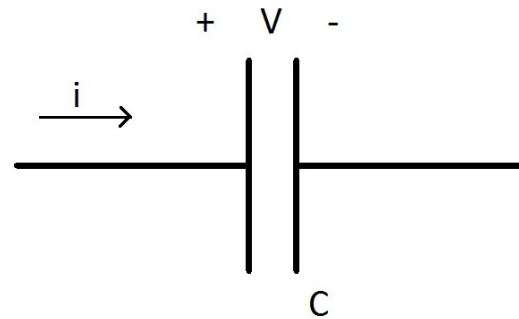
- $i(t) = C \frac{dv(t)}{dt}$
- $V(t) = \left( \int_{t_0}^t \frac{i(t)}{C} \right) + V(t_0)$




Inductor

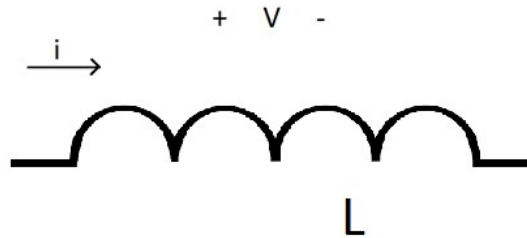- $V(t) = L \frac{di(t)}{dt}$
- $i(t) = \left( \int_{t_0}^t \frac{V(t)}{L} \right) + i(t_0)$



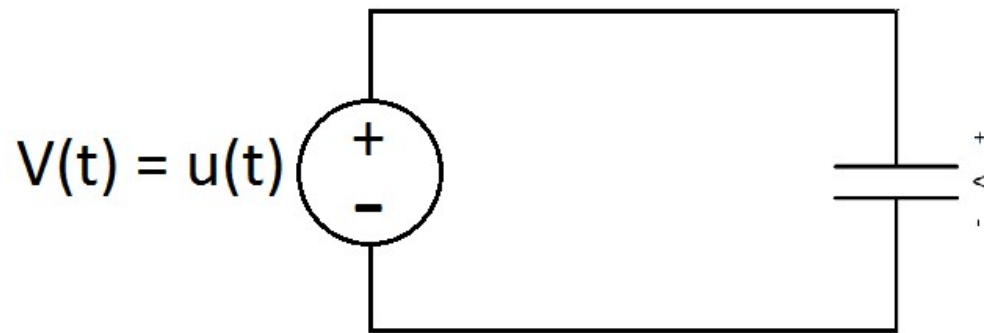



“unhealthy” differentiator circuit.

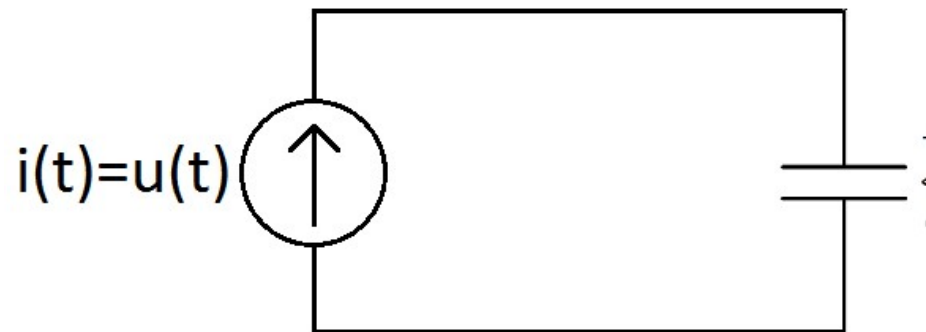


integrator


Capacitor

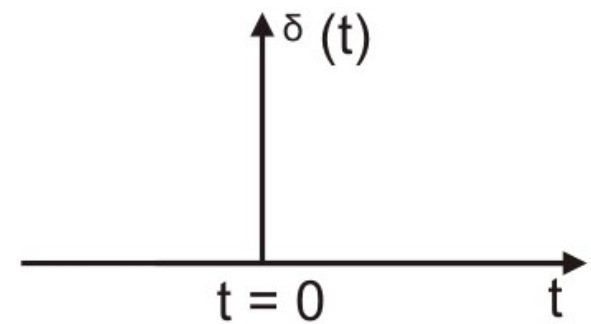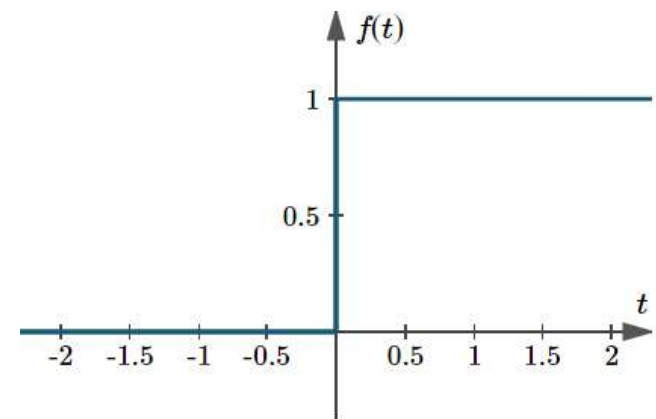- $i(t) = C \frac{dv(t)}{dt}$
- $V(t) = \left( \int_{t_0}^t \frac{i(t)}{C} \right) + V(t_0)$



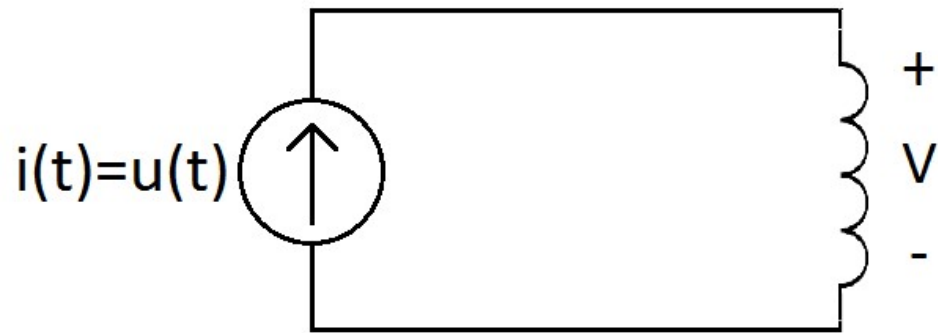


“unhealthy” differentiator circuit.

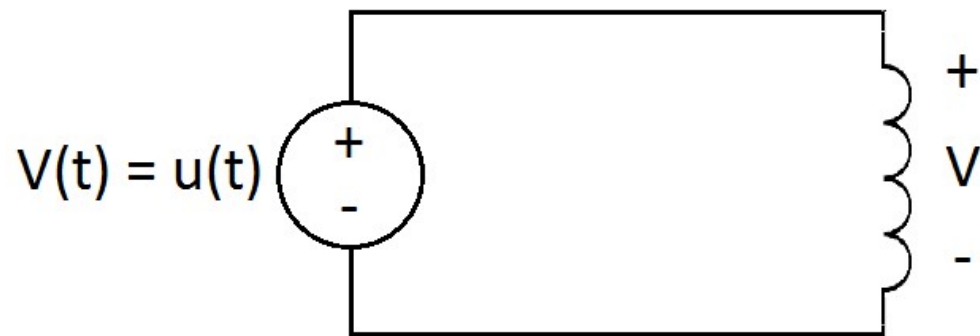


integrator

$$V(t) = L \frac{di(t)}{dt}$$

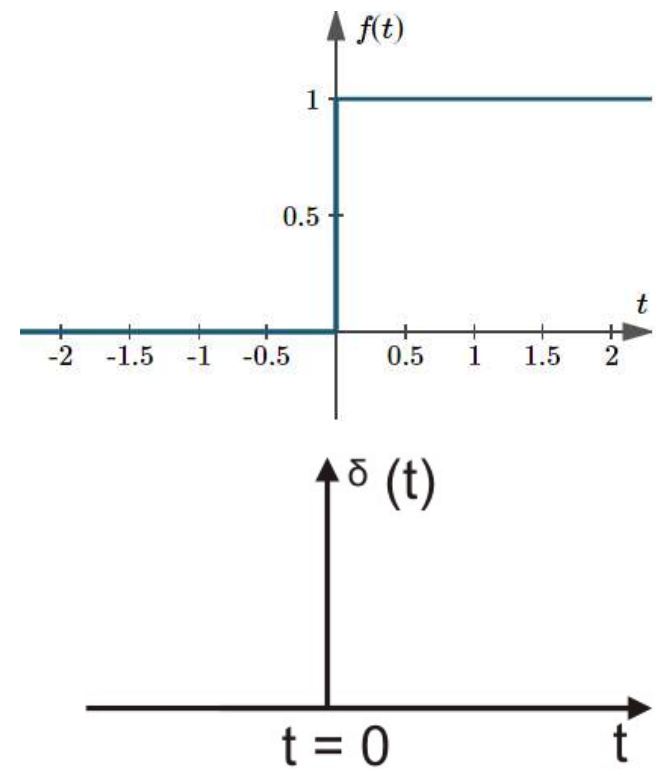
$$i(t) = \left( \int_{t_0}^t \frac{V(t)}{L} \right) + i(t_0)$$



- Op-amp differentiator

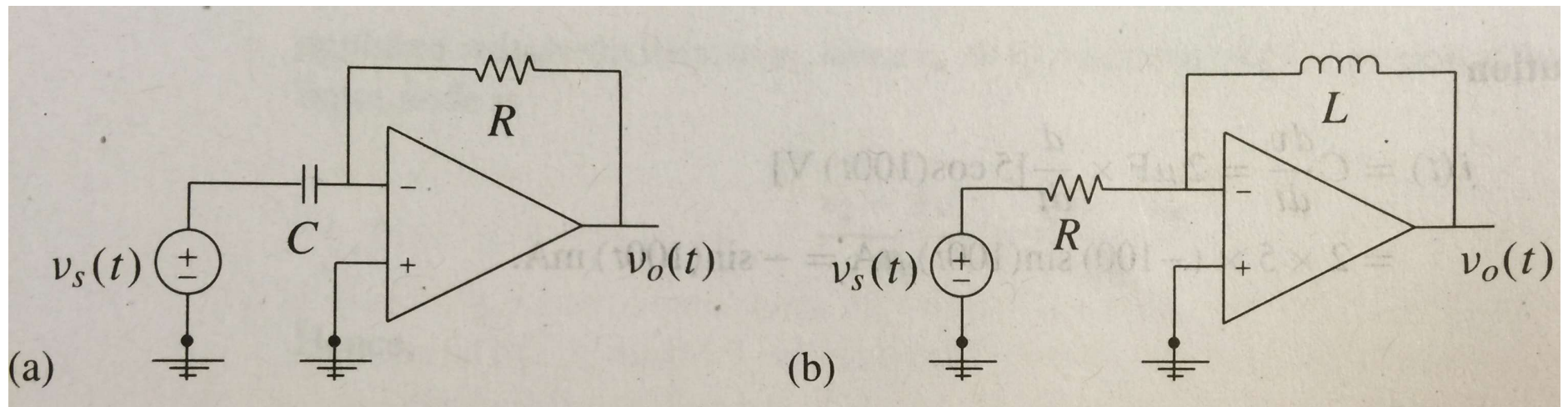

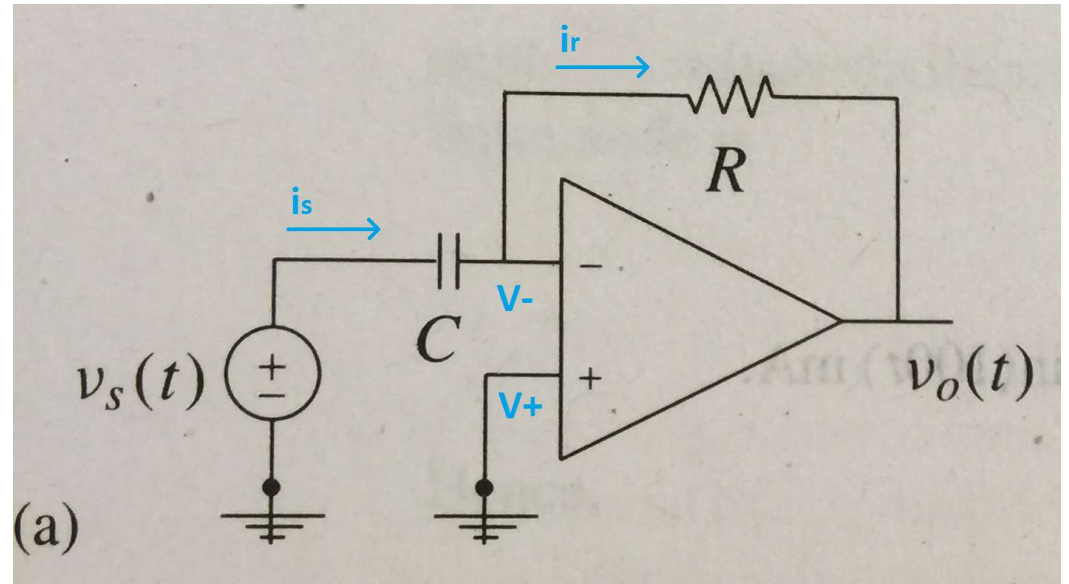- $V_- = V_+ = 0$
- $i_s = C \frac{d(V_s - V_-)}{dt} = C \frac{dV_s}{dt}$
- $i_s = i_r$
- $V_o = V_- - i_r R = -RC \frac{dV_s}{dt}$




Capacitor

$$i(t) = C \frac{dv(t)}{dt}$$

$$V(t) = \left( \int_{t_0}^t \frac{i(t)}{C} \right) + V(t_0)$$

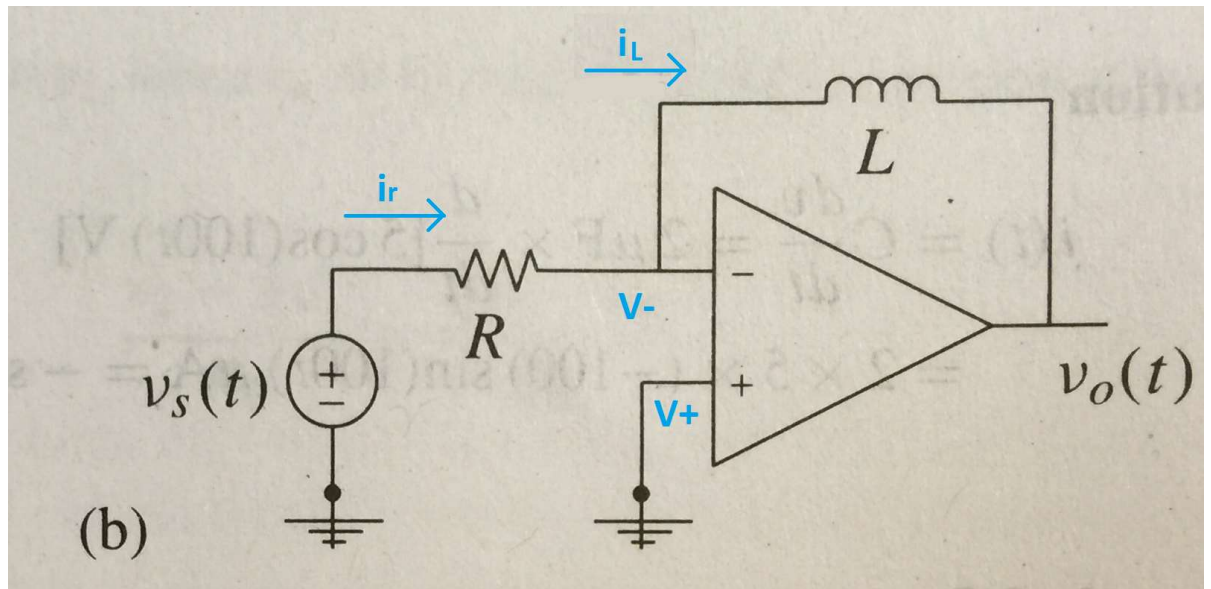- $V_- = V_+ = 0$
- $i_r = \frac{V_s}{R}$
- $i_L = i_r$
- $V_- - V_o = L \frac{di_L}{dt}$
- $V_o = -\frac{L}{R} \frac{dV_s}{dt}$




Inductor


$$V(t) = L \frac{di(t)}{dt}$$

$$i(t) = \left( \int_{t_0}^t \frac{V(t)}{L} \right) + i(t_0)$$

- Op-amp integrator

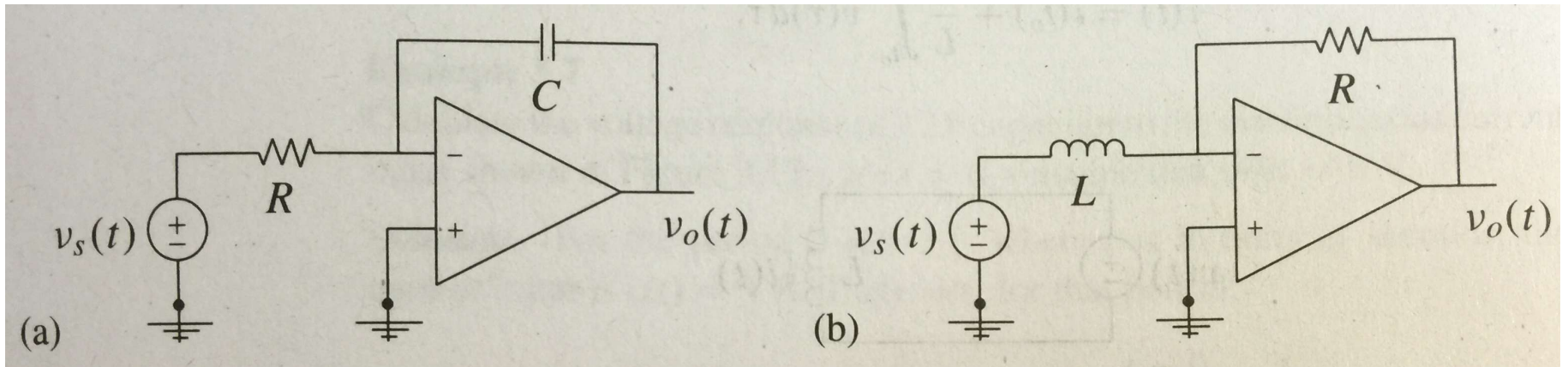

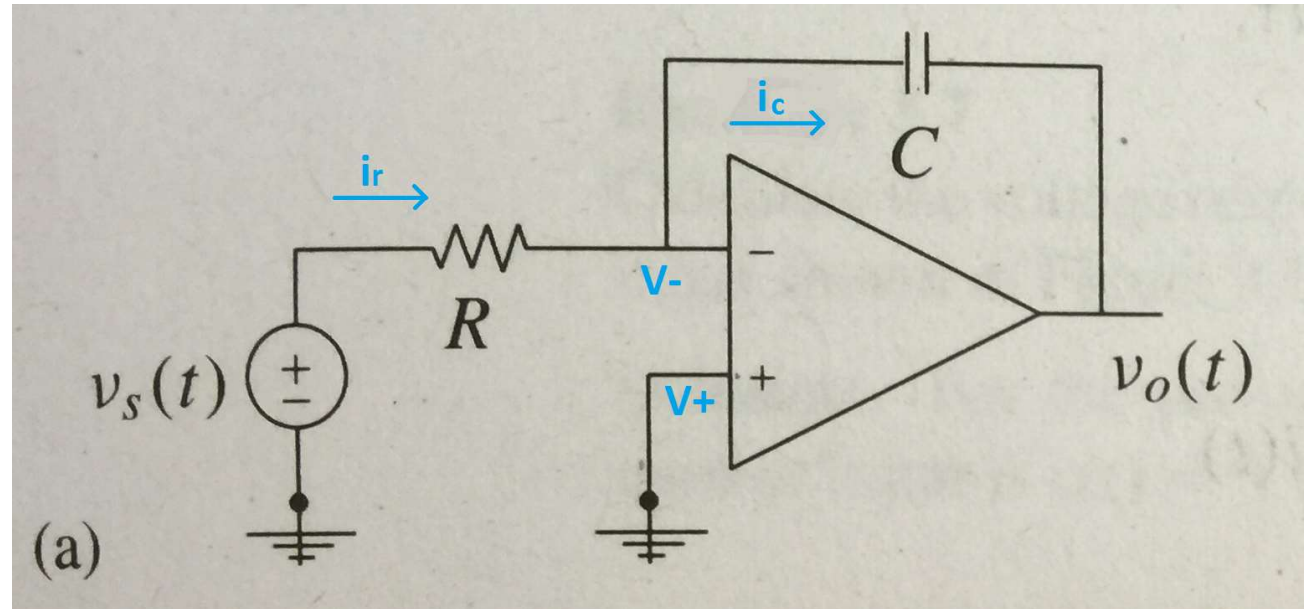- $V_- = V_+ = 0$
- $i_r = \frac{V_s}{R}$
- $i_c = i_r$
- $V_- - V_o = \left( \int_{t_0}^t \frac{i_c(t)}{C} \right) + V_c(t_0)$
- $V_o = - \left( \int_{t_0}^t \frac{V_s(t)}{RC} \right) - V_c(t_0)$




$$i(t) = C \frac{dv(t)}{dt}$$

$$V(t) = \left( \int_{t_0}^t \frac{i(t)}{C} \right) + V(t_0)$$



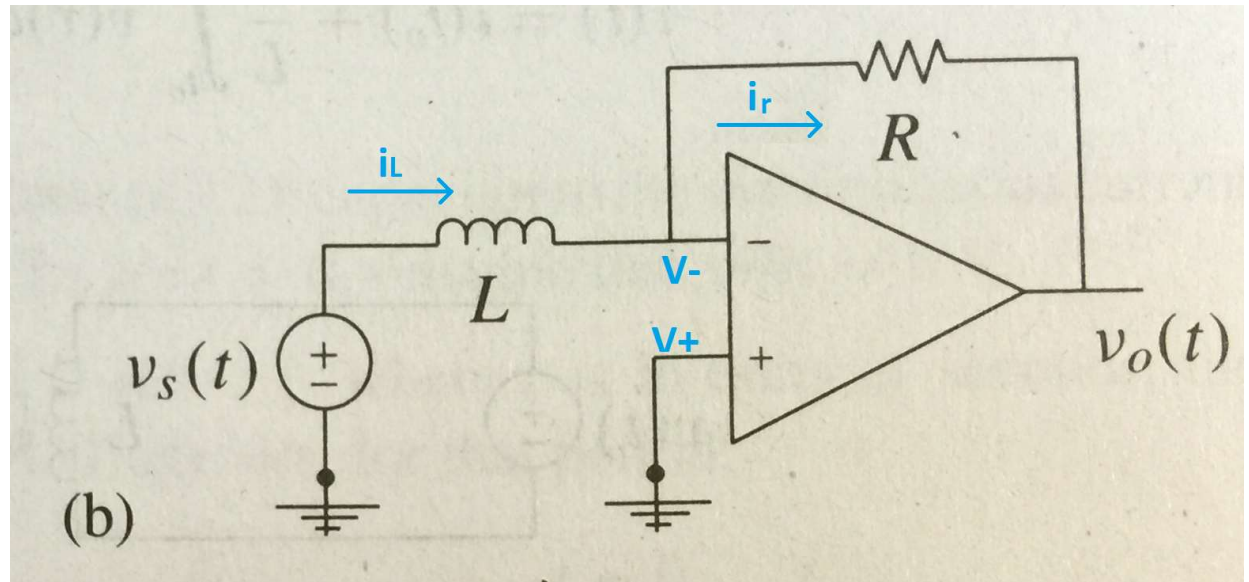- $V_- = V_+ = 0$
- $i_L = \left( \int_{t_0}^t \frac{V_s(t)}{L} \right) + i(t_0)$
- $i_L = i_r$
- $V_- - V_o = i_r R = \left( \left( \int_{t_0}^t \frac{V_s(t)}{L} \right) + i(t_0) \right) R$
- $V_o = - \left( \left( \int_{t_0}^t \frac{V_s(t)}{L} \right) + i(t_0) \right) R$



$$V(t) = L \frac{di(t)}{dt}$$

$$i(t) = \left( \int_{t_0}^t \frac{V(t)}{L} \right) + i(t_0)$$

## 3.3 Linearity, Time Invariance, & LTI System


- Linearity

- $y(t) = y(t_0) + \int_{t_0}^t f(\tau) d\tau$

Zero-input response

Zero-state response

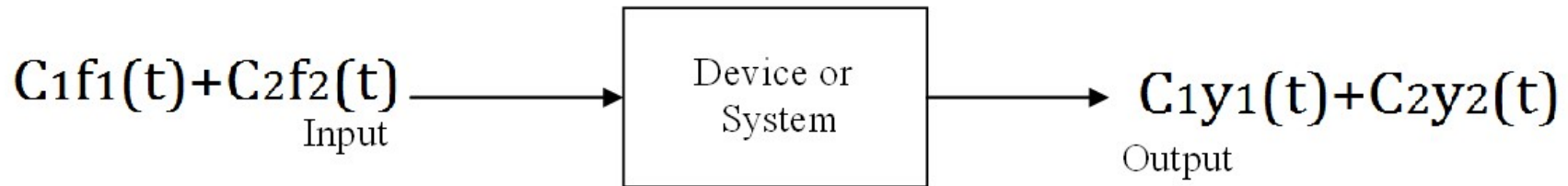- A system is said to be linear if its output is a sum of distinct zero-input and zero-state responses that vary linearly with the initial state of the system and linearly with the system input, respectively.




- How to decide whether linear or not?
- Assume
  - $f_1(t) \rightarrow y_1(t)$
  - $f_2(t) \rightarrow y_2(t)$
  - $f_3(t) = C_1f_1(t) + C_2f_2(t)$
- If  $y_3(t) = C_1y_1(t) + C_2y_2(t)$  holds true, then we say the system is linear

- E.g. Verify  $y(t) = \int_{t_0}^t f(t)dt$  is linear.
- Assume
  - $f_1(t) \rightarrow y_1(t), y_1(t) = \int_{t_0}^t f_1(t)dt$
  - $f_2(t) \rightarrow y_2(t), y_2(t) = \int_{t_0}^t f_2(t)dt$
  - $f_3(t) = C_1 f_1(t) + C_2 f_2(t)$
- $y_3(t) = \int_{t_0}^t f_3(t)dt = \int_{t_0}^t (C_1 f_1(t) + C_2 f_2(t))dt$ 

$$= C_1 \int_{t_0}^t f_1(t)dt + C_2 \int_{t_0}^t f_2(t)dt$$

$$= C_1 y_1(t) + C_2 y_2(t)$$
- That this system is linear is hereby proved.

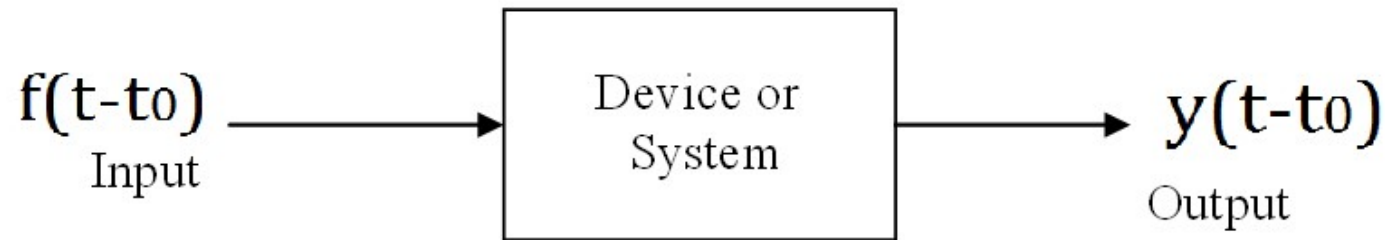- E.g. Verify  $y(t) = f^2(t)$  is not linear.
- Assume
  - $f_1(t) \rightarrow y_1(t), y_1(t) = f_1^2(t)$
  - $f_2(t) \rightarrow y_2(t), y_2(t) = f_2^2(t)$
  - $f_3(t) = C_1 f_1(t) + C_2 f_2(t)$
- $y_3(t) = f_3^2(t) = (C_1 f_1(t) + C_2 f_2(t))^2$   
 $\neq C_1 y_1(t) + C_2 y_2(t)$
- That this system is not linear is hereby proved.



- Time-invariance
- Delayed inputs cause equally delayed outputs

- How to decide whether time-invariant or not?
- Assume
  - $f_1(t) \rightarrow y_1(t)$
  - $f_2(t) = f_1(t - t_0)$
  - $f_2(t) \rightarrow y_2(t)$
- If  $y_2(t) = y_1(t - t_0)$  holds true, then we say the system is time-invariant

- E.g. Verify  $y(t) = \int_{t_0}^t f(t)dt$  is time-invariant.

- Assume

- $f_1(t) \rightarrow y_1(t), y_1(t) = \int_{t_0}^t f_1(t)$

- $f_2(t) = f_1(t - t_0)$

- $f_2(t) \rightarrow y_2(t)$

- $y_2(t) = \int_{t_0}^t f_2(t)dt = \int_{t_0}^t f_1(t - t_0)dt$

$$y_1(t - t_0) = \int_{t_0}^t f_1(t - t_0)dt$$

$$y_2(t) = y_1(t - t_0)$$

That this system is time-invariant is hereby proved.



- E.g. Verify  $y(t) = \int_{t_0}^t f(3 - t)dt$  is not time-invariant.

- Assume

- $f_1(t) \rightarrow y_1(t), y_1(t) = \int_{t_0}^t f_1(3 - t)$

- $f_2(t) = f_1(t - t_0)$

- $f_2(t) \rightarrow y_2(t)$

- $y_2(t) = \int_{t_0}^t f_2(t)dt = \int_{t_0}^t f_1((3 - t) - t_0)dt$

$$y_1(t - t_0) = \int_{t_0}^t f_1(3 - (t - t_0))$$

$$y_2(t) \neq y_1(t - t_0)$$


That this system is not time-invariant is hereby proved.

## 3.4 First-order RC & RL Circuits

- Capacitor and inductor


Capacitor

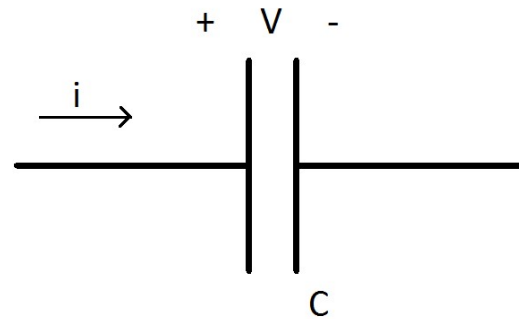- $i(t) = C \frac{dv(t)}{dt}$
- $V(t) = \left( \int_{t_0}^t \frac{i(t)}{C} \right) + V(t_0)$




Inductor

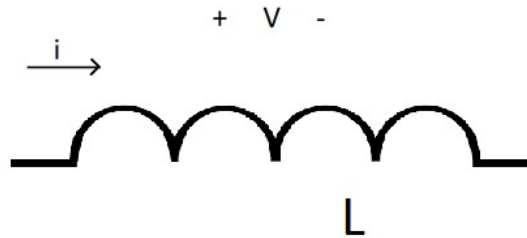- $V(t) = L \frac{di(t)}{dt}$
- $i(t) = \left( \int_{t_0}^t \frac{V(t)}{L} \right) + i(t_0)$



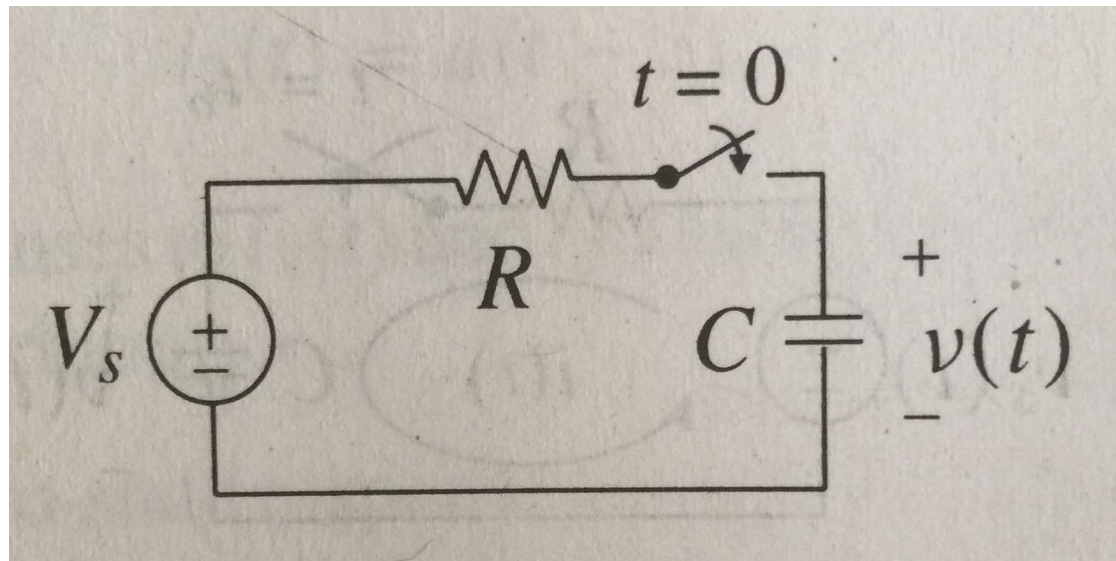- RC-circuit response to constant sources




- KVL

- $V_s = V_r + V$

- $V_s = iR + V$

- $V_s = \left( C \frac{dv(t)}{dt} \right) R + V$

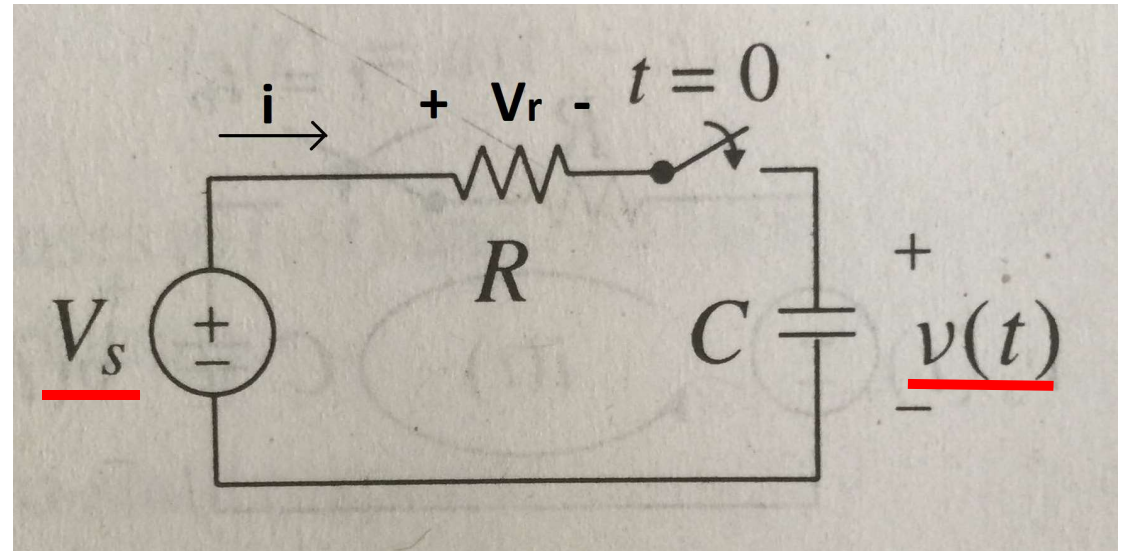- $\frac{dv}{dt} + \frac{1}{RC} v = \frac{1}{RC} V_s$



$$i(t) = C \frac{dv(t)}{dt}$$


$$V(t) = \left( \int_{t_0}^t \frac{i(t)}{C} \right) + V(t_0)$$

- $\frac{dv}{dt} + \frac{1}{RC} v = \frac{1}{RC} V_s$

- $v = A e^{-\frac{t}{RC}} + V_s$

- When  $t = 0$ ,  $v(0) = v(0^-) = A + V_s$

- $A = v(0^-) - V_s$

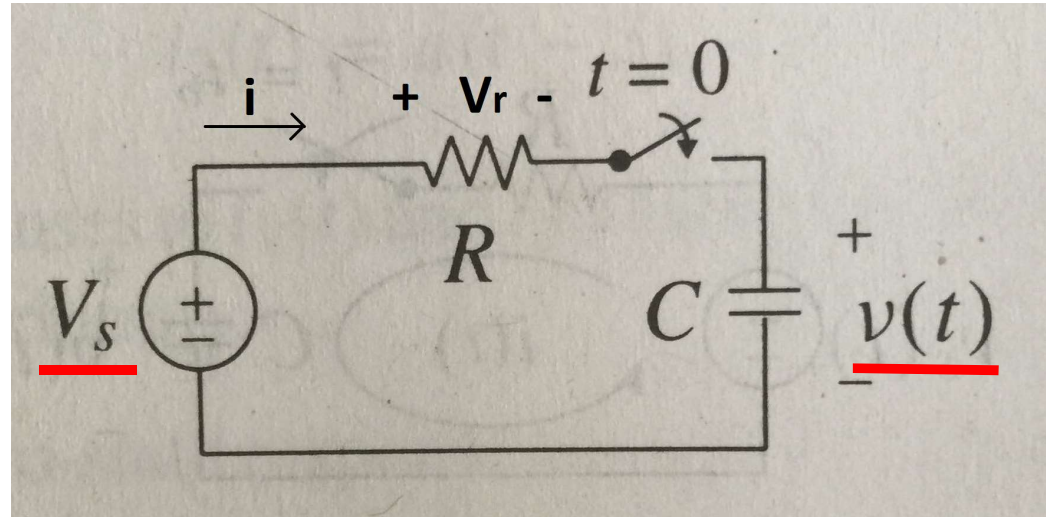

## 3.3 Linearity, Time Invariance, & LTI System


- Linearity

The diagram shows the equation  $y(t) = y(t_0) + \int_{t_0}^t f(\tau) d\tau$  enclosed in a red rectangular box. Below the box, the text "Zero-input response" is aligned under  $y(t_0)$  and "Zero-state response" is aligned under the integral term. A blue arrow points from  $y(t_0)$  down to "Zero-input response", and another blue arrow points from the integral term down to "Zero-state response".

$$y(t) = y(t_0) + \int_{t_0}^t f(\tau) d\tau$$

Zero-input response                      Zero-state response

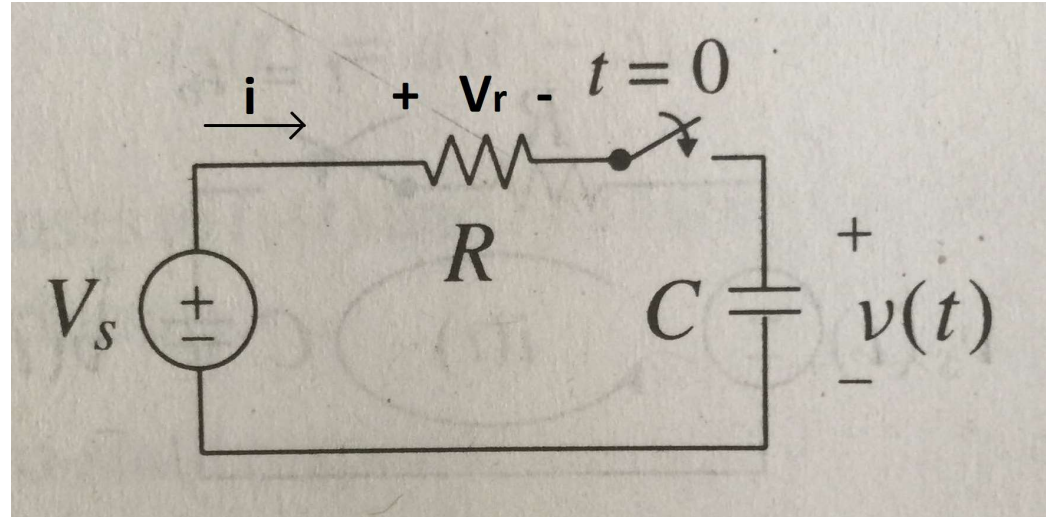- A system is said to be linear if its output is a sum of distinct zero-input and zero-state responses that vary linearly with the initial state of the system and linearly with the system input, respectively.



- $\frac{dv}{dt} + \frac{1}{RC}v = \frac{1}{RC}V_s$

- $v = Ae^{-\frac{t}{RC}} + V_s$


- $A = v(0-) - V_s$

$$\left. \begin{array}{l} \bullet \\ \bullet \\ \bullet \end{array} \right\} \rightarrow v = (v(0-) - V_s)e^{-\frac{t}{RC}} + V_s$$

$$v = e^{-\frac{t}{RC}}v(0-) + (1 - e^{-\frac{t}{RC}})V_s$$

$$v = v_{\text{zero-input}} + v_{\text{zero-state}}$$

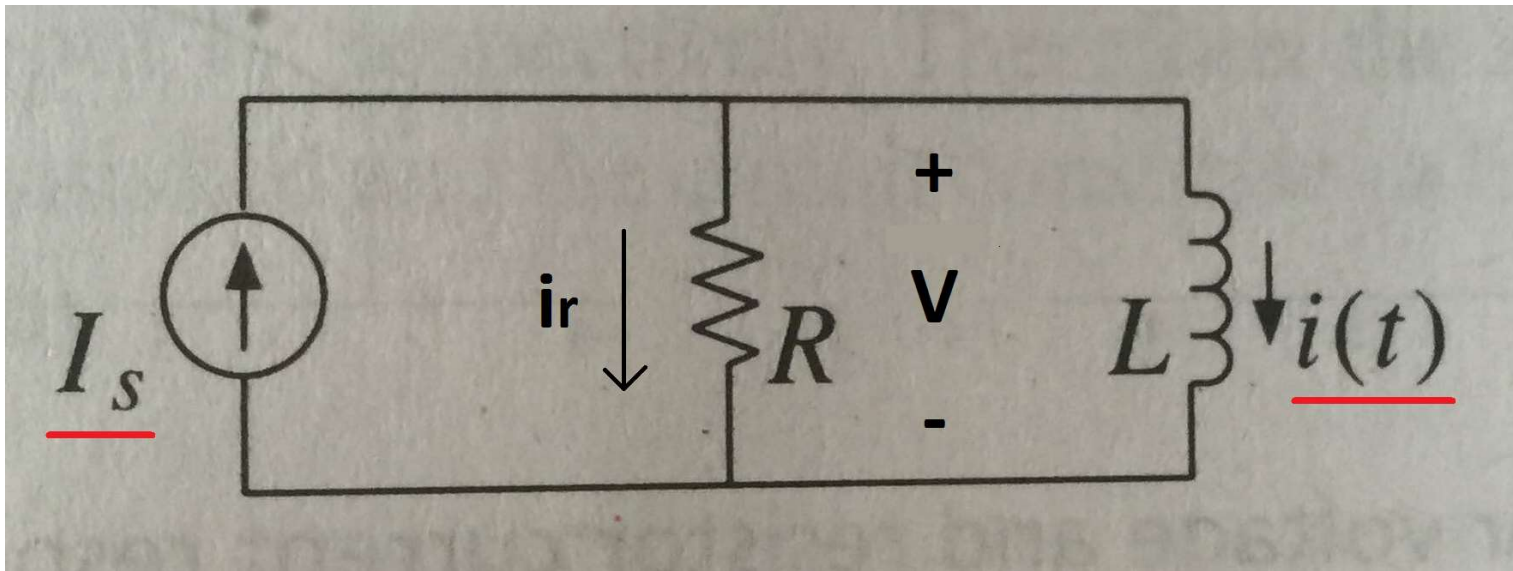- RL-circuit response to constant sources






- KCL

- $I_s = i_r + i$

- $I_s = \frac{V}{R} + i$

- $I_s = \frac{(L \frac{di(t)}{dt})}{R} + i$

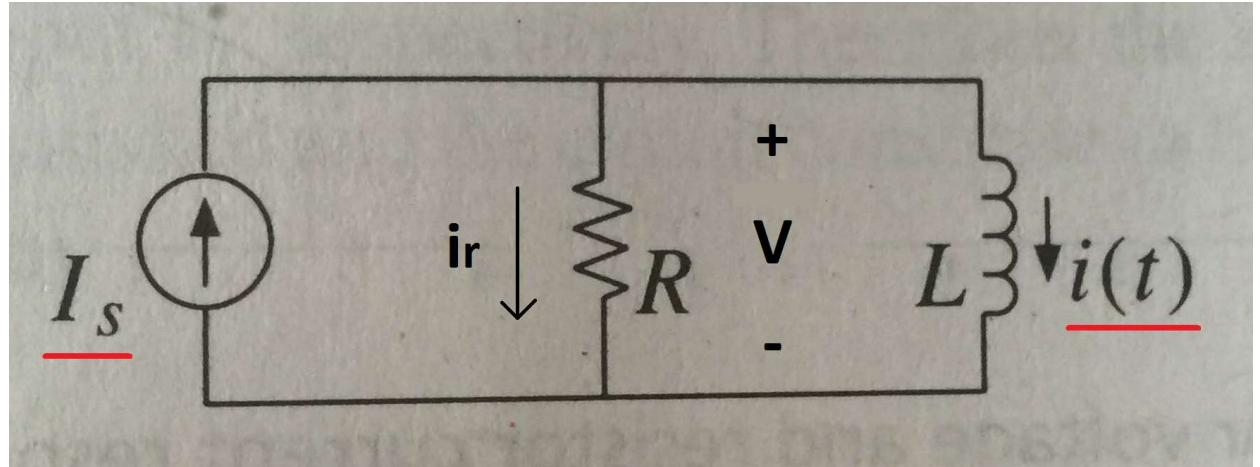
- $\frac{di}{dt} + \frac{R}{L} i(t) = \frac{R}{L} I_s$



$$V(t) = L \frac{di(t)}{dt}$$

$$i(t) = \left( \int_{t_0}^t \frac{V(t)}{L} \right) + i(t_0)$$

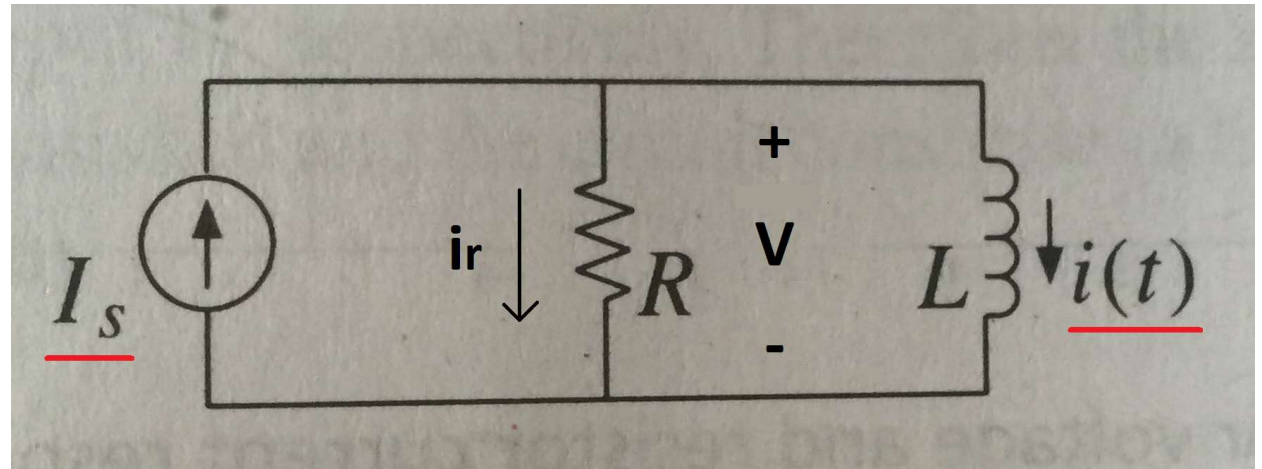- $\frac{di}{dt} + \frac{R}{L}i(t) = \frac{R}{L}I_s$



- $i = (i(0-) - I_s)e^{-\frac{t}{L/R}} + I_s$
- $i = e^{-\frac{t}{L/R}}i(0-) + (1 - e^{-\frac{t}{L/R}})I_s$


$$i = i_{\text{zero-input}} + i_{\text{zero-state}}$$

Two blue arrows point from the terms in the equation above to the corresponding terms in the equation below: one from  $i(0-)$  to  $i_{\text{zero-input}}$  and one from  $(1 - e^{-\frac{t}{L/R}})I_s$  to  $i_{\text{zero-state}}$ .

- Initial energy


- $E_C = \frac{1}{2} CV^2$

- $E_C = \frac{1}{2} CV(0-)^2$

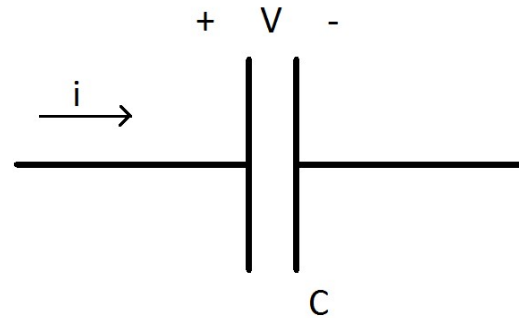


- $E_L = \frac{1}{2} LI^2$


- $E_L = \frac{1}{2} LI(0-)^2$

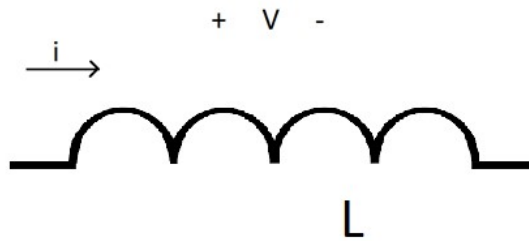

- Steady state

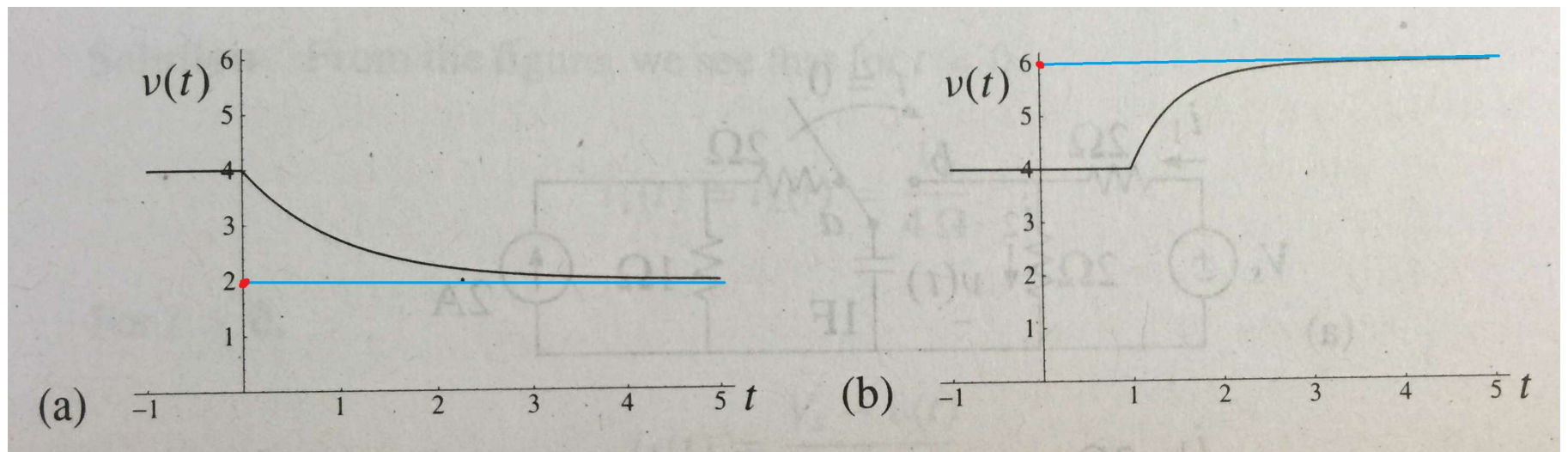


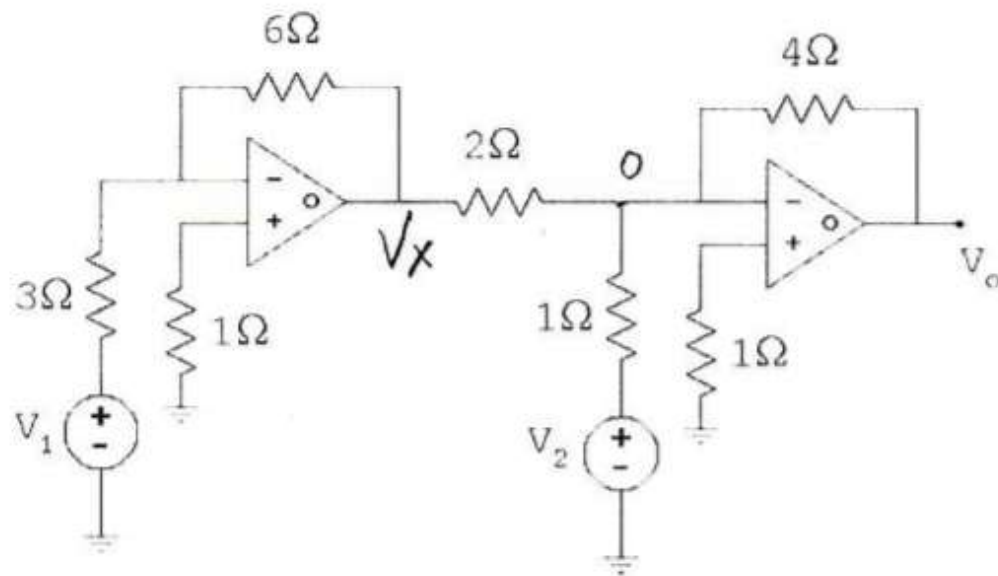4. (10 pts) In the following circuit, assuming linear operation and ideal op-amp approximation, express the output voltage  $V_o$ , in terms of  $V_1$  and  $V_2$ .



$$V_o = \underline{4V_1 - 4V_2}$$


**Problem 4** (25 points)

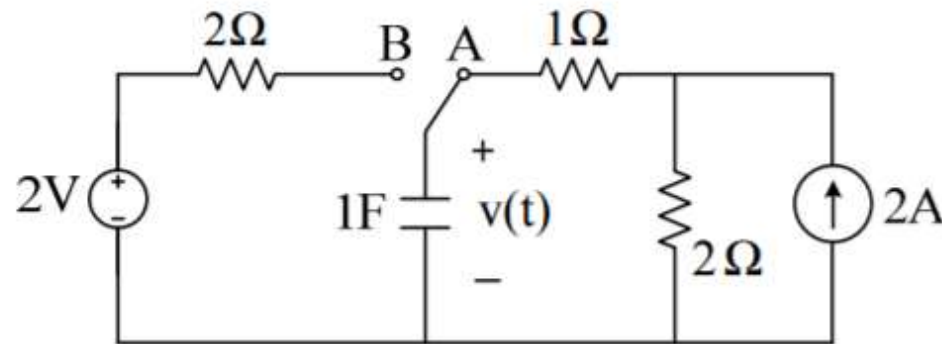

Assume the switch has been in position A for a long time. It moves to position B at  $t = 0$ .

- a) (5 points) Write the 1<sup>st</sup> order ODE of  $v(t)$  for  $t > 0$ .
- b) (3 points) Find the initial value of  $v(t)$  at  $t = 0^-$ .
- c) (8 points) Solve  $v(t)$  for  $t > 0$ .
- d) (3 points) What is the zero input component of  $v(t)$ ?
- e) (3 points) What is the zero state component of  $v(t)$ ?
- f) (3 points) What is the steady state value of  $v(t)$  for  $t > 0$ ?

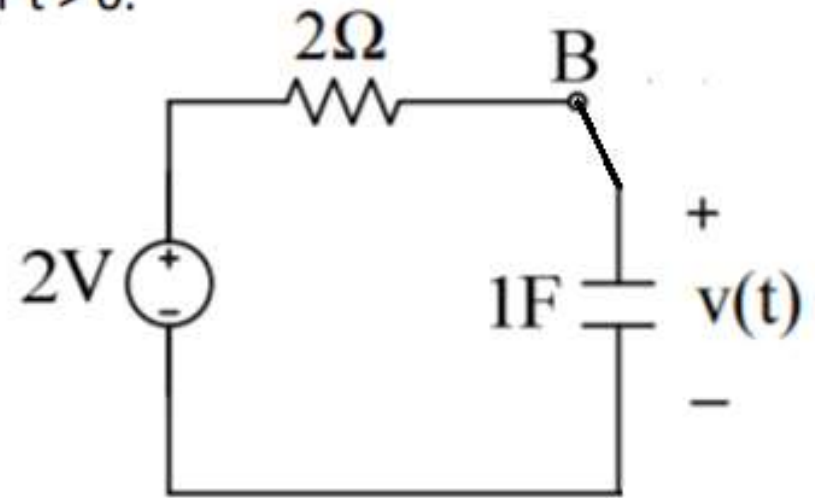
a) (5 points) Write the 1<sup>st</sup> order ODE of  $v(t)$  for  $t > 0$ .



$$i(t) = C \frac{dv(t)}{dt}$$

$$V(t) = \left( \int_{t_0}^t \frac{i(t)}{C} \right) + V(t_0)$$

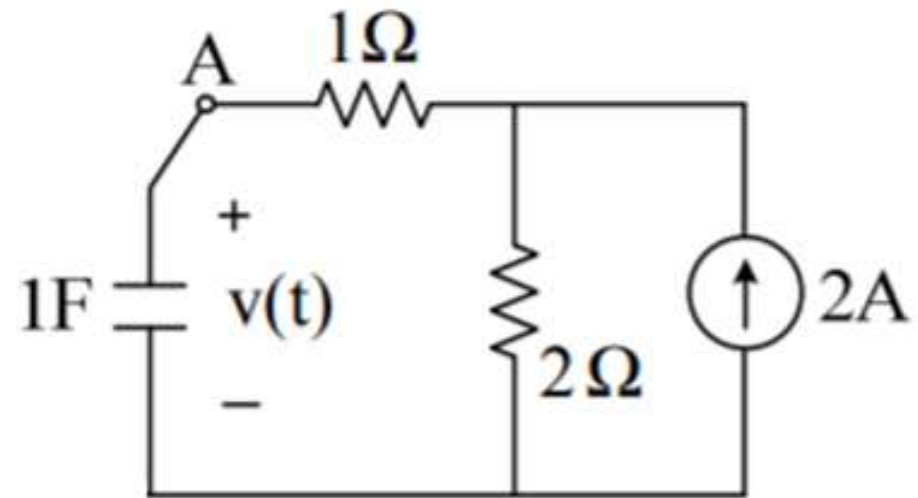**b)** (3 points) Find the initial value of  $v(t)$  at  $t = 0^-$ .




$$i(t) = C \frac{dv(t)}{dt}$$

$$V(t) = \left( \int_{t_0}^t \frac{i(t)}{C} \right) + V(t_0)$$




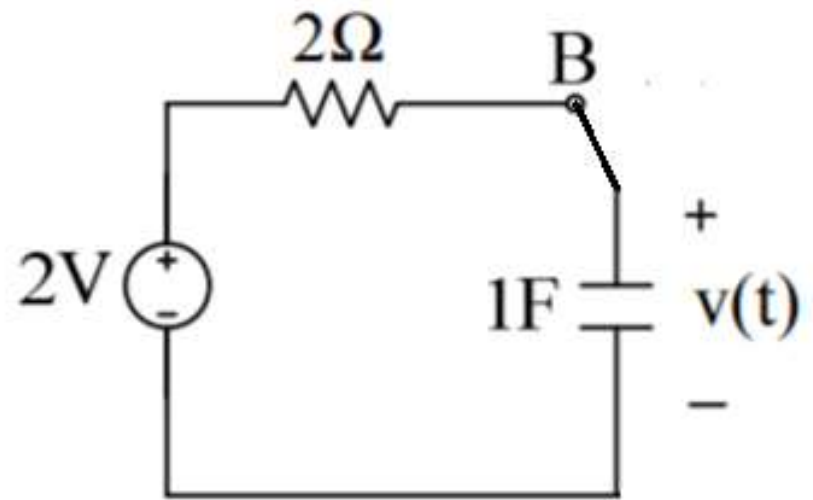c) (8 points) Solve  $v(t)$  for  $t > 0$ .

- $\frac{dv}{dt} + \frac{1}{2}v = 1$
- $v_{0-} = 4$
- $v = Ae^{-\frac{t}{RC}} + V_s$
- $A = v(0-) - V_s$



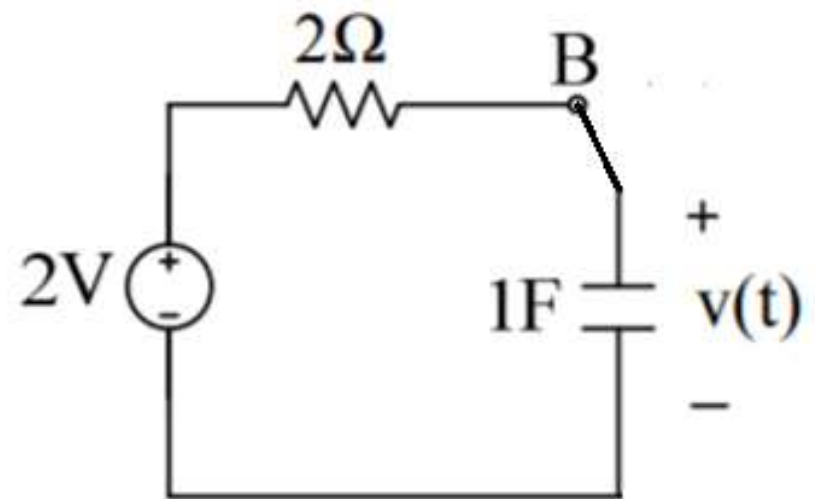c) (8 points) Solve  $v(t)$  for  $t > 0$ .



- $\frac{dv}{dt} + \frac{1}{2}v = 1$


- $v_{0-} = 4$

- $v = Ae^{-\frac{t}{RC}} + V_s$


- $A = v(0-) - V_s$

**d)** (3 points) What is the zero input component of  $v(t)$ ?

**e)** (3 points) What is the zero state component of  $v(t)$ ?
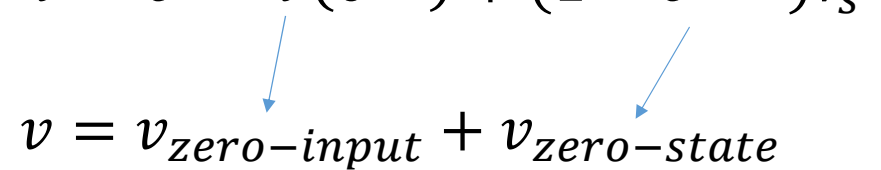
$$v = (v(0-) - V_s)e^{-\frac{t}{RC}} + V_s$$
$$v = e^{-\frac{t}{RC}}v(0-) + (1 - e^{-\frac{t}{RC}})V_s$$
$$v = v_{\text{zero-input}} + v_{\text{zero-state}}$$

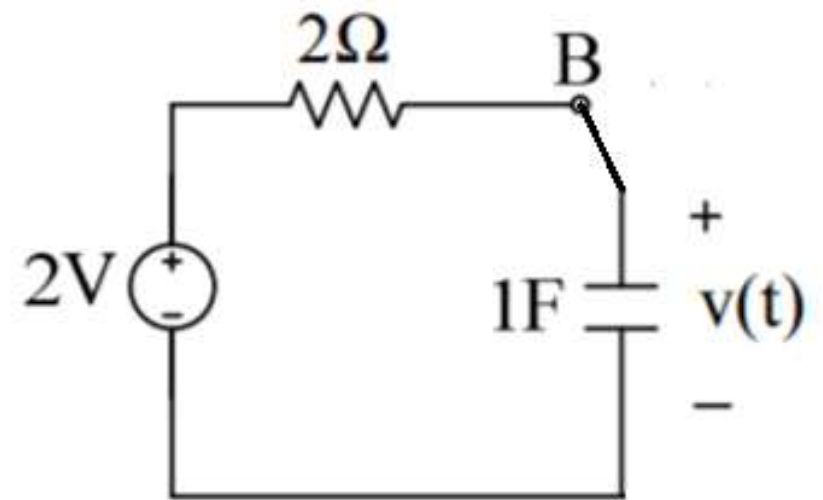
**f)** (3 points) What is the steady state value of  $v(t)$  for  $t > 0$ ?



Questions?

